
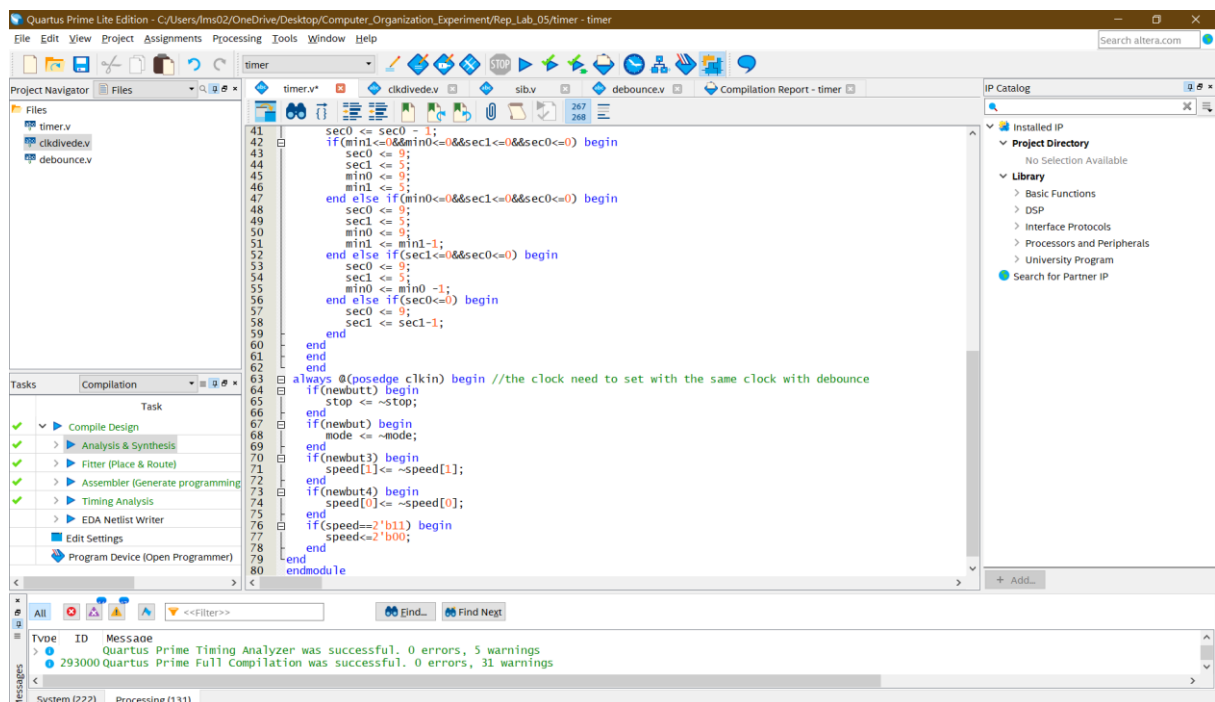




Lab 5 Sequence and Control; Digital clock design


Description:

In this lab, we are going to make a timer, which has a lot of function to make it count faster, slower, count up, and count down. Furthermore, we also need a button to make the timer stop and start.

Code:

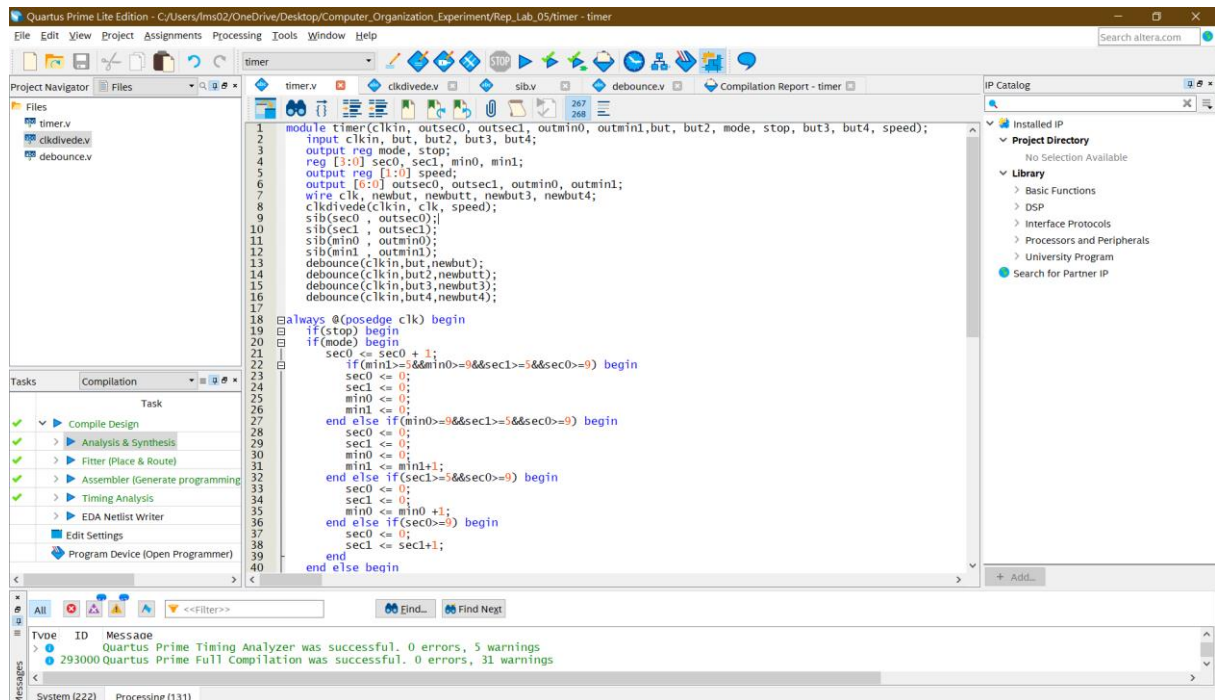

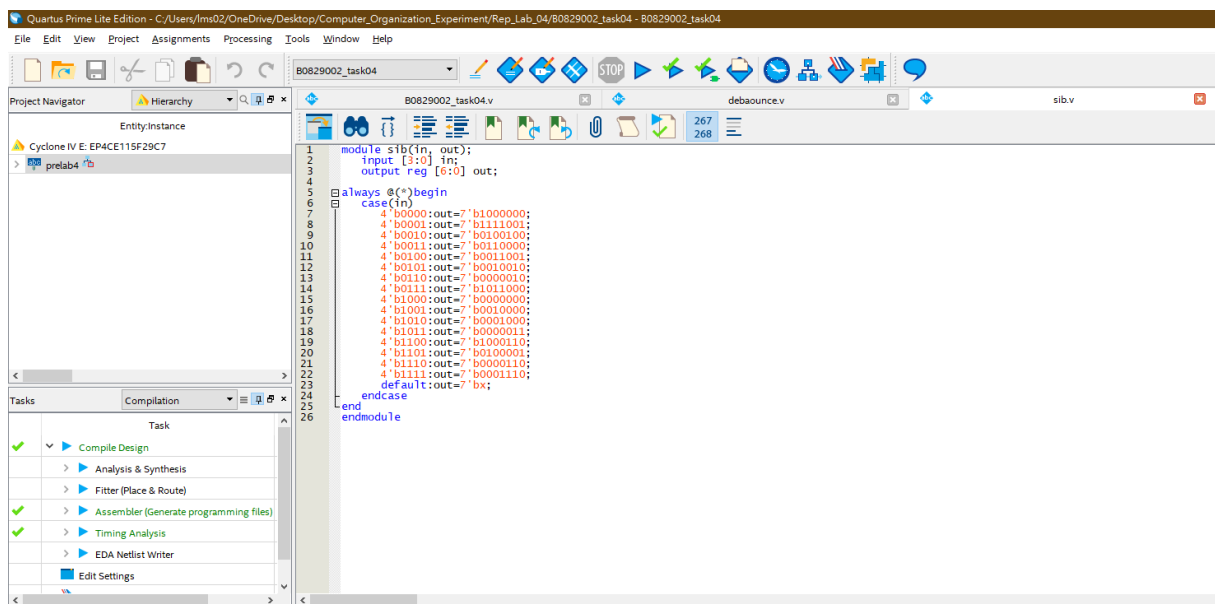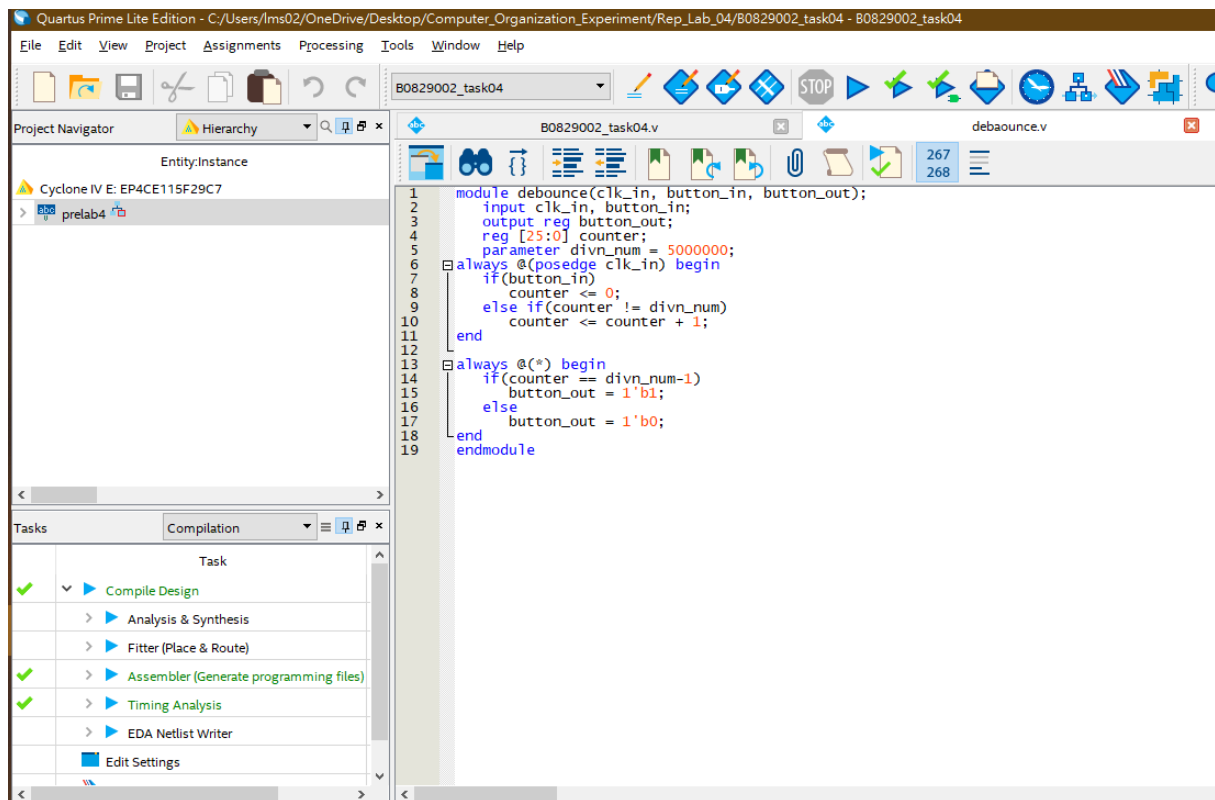

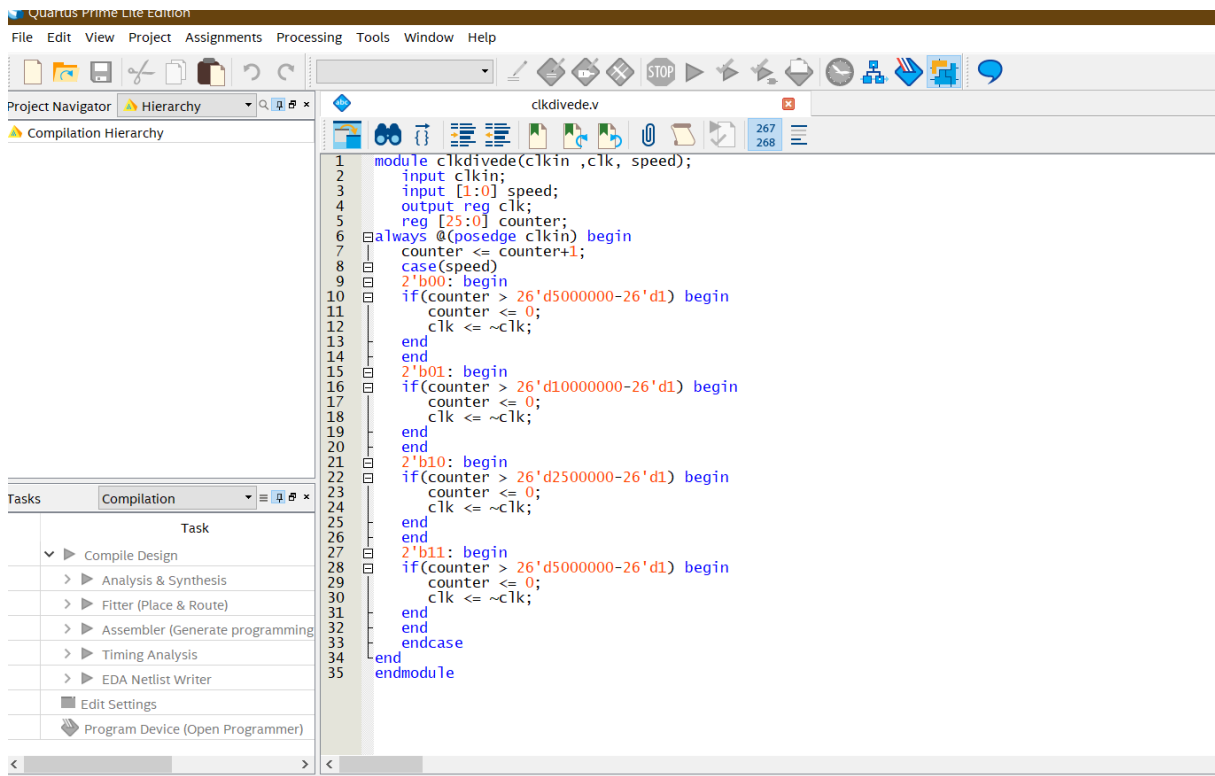

RTL Design:



RTL.pdf

Pin planer:

The screenshot displays the Pin Planner interface. The main window shows a top-level view of the pin assignment table. The table lists the node name, direction, location, I/O bank, VREF group, filter location, I/O standard, reserved, current strength, slew rate, differential pair, and I/O preservation.

Node Name	Direction	Location	I/O Bank	VREF Group	Filter Location	I/O Standard	Reserved	Current Strength	Slew Rate	Differential Pair	I/O Preservation
outmin0[4]	Output	PIN_Y26	5	B5_N1	PIN_Y26	2.5 V		8mA (default)	2 (default)		
outmin0[3]	Output	PIN_Y26	5	B5_N1	PIN_Y26	2.5 V		8mA (default)	2 (default)		
outmin0[2]	Output	PIN_Y25	5	B5_N1	PIN_Y25	2.5 V		8mA (default)	2 (default)		
outmin0[1]	Output	PIN_AA26	5	B5_N1	PIN_AA26	2.5 V		8mA (default)	2 (default)		
outmin0[0]	Output	PIN_AA25	5	B5_N1	PIN_AA25	2.5 V		8mA (default)	2 (default)		
outmin1[6]	Output	PIN_Y19	4	B4_N0	PIN_Y19	2.5 V		8mA (default)	2 (default)		
outmin1[5]	Output	PIN_AF23	4	B4_N0	PIN_AF23	2.5 V		8mA (default)	2 (default)		
outmin1[4]	Output	PIN_AD24	4	B4_N0	PIN_AD24	2.5 V		8mA (default)	2 (default)		
outmin1[3]	Output	PIN_AA21	4	B4_N0	PIN_AA21	2.5 V		8mA (default)	2 (default)		
outmin1[2]	Output	PIN_AB20	4	B4_N0	PIN_AB20	2.5 V		8mA (default)	2 (default)		
outmin1[1]	Output	PIN_U21	5	B5_N0	PIN_U21	2.5 V		8mA (default)	2 (default)		
outmin1[0]	Output	PIN_V21	5	B5_N1	PIN_V21	2.5 V		8mA (default)	2 (default)		
outsec0[6]	Output	PIN_H22	6	B6_N0	PIN_H22	2.5 V		8mA (default)	2 (default)		
outsec0[5]	Output	PIN_J22	6	B6_N0	PIN_J22	2.5 V		8mA (default)	2 (default)		
outsec0[4]	Output	PIN_L25	6	B6_N1	PIN_L25	2.5 V		8mA (default)	2 (default)		
outsec0[3]	Output	PIN_L26	6	B6_N1	PIN_L26	2.5 V		8mA (default)	2 (default)		
outsec0[2]	Output	PIN_E17	7	B7_N2	PIN_E17	2.5 V		8mA (default)	2 (default)		
outsec0[1]	Output	PIN_F22	7	B7_N0	PIN_F22	2.5 V		8mA (default)	2 (default)		
outsec0[0]	Output	PIN_G18	7	B7_N2	PIN_G18	2.5 V		8mA (default)	2 (default)		
outsec1[6]	Output	PIN_U24	5	B5_N0	PIN_U24	2.5 V		8mA (default)	2 (default)		
outsec1[5]	Output	PIN_U23	5	B5_N1	PIN_U23	2.5 V		8mA (default)	2 (default)		
outsec1[4]	Output	PIN_W25	5	B5_N1	PIN_W25	2.5 V		8mA (default)	2 (default)		
outsec1[3]	Output	PIN_W22	5	B5_N0	PIN_W22	2.5 V		8mA (default)	2 (default)		
outsec1[2]	Output	PIN_W21	5	B5_N1	PIN_W21	2.5 V		8mA (default)	2 (default)		
outsec1[1]	Output	PIN_Y22	5	B5_N0	PIN_Y22	2.5 V		8mA (default)	2 (default)		
outsec1[0]	Output	PIN_M24	6	B6_N2	PIN_M24	2.5 V		8mA (default)	2 (default)		
speed[1]	Output	PIN_F21	7	B7_N0	PIN_F21	2.5 V		8mA (default)	2 (default)		
speed[0]	Output	PIN_E19	7	B7_N0	PIN_E19	2.5 V		8mA (default)	2 (default)		
stop	Output	PIN_F19	7	B7_N0	PIN_F19	2.5 V		8mA (default)	2 (default)		

Explanation:

For count up, we just determine count to 9+1 or 5+1 need the back signal reset to zero and the next signal add 1. For counting down, we use another method to determine when it count to 0-1 and the back signal will reset to 9 or 5. And the front signal will minus 1.

If we need to use start and stop, it is easy to use control unit to achieve the action. We can use a if-else determination when $stop == 1$, then the timer stop to count and $stop == 0$, the timer start counting.

Discussion for difficulties and problems:

Last but not least, when we face to the speed of counting, we can divide the clock trigger to achieve the faster 2x or 0.5x times (using n-bit counter or module-n counter), then we also using the control unit (if-else statement) to control the state of speed.

The most difficult problem I met is, when I using the different clock trigger for state determination and changing, it will happen that the trigger of clock for state changing and debounce.v is different, thus the state will not change. It also lead to most of control unit can not take action because when the clock trigger the state of button has changed and there is no clock trigger or different signal yet.

Therefore, the solution is using the same clock for all of the non-blocking function.