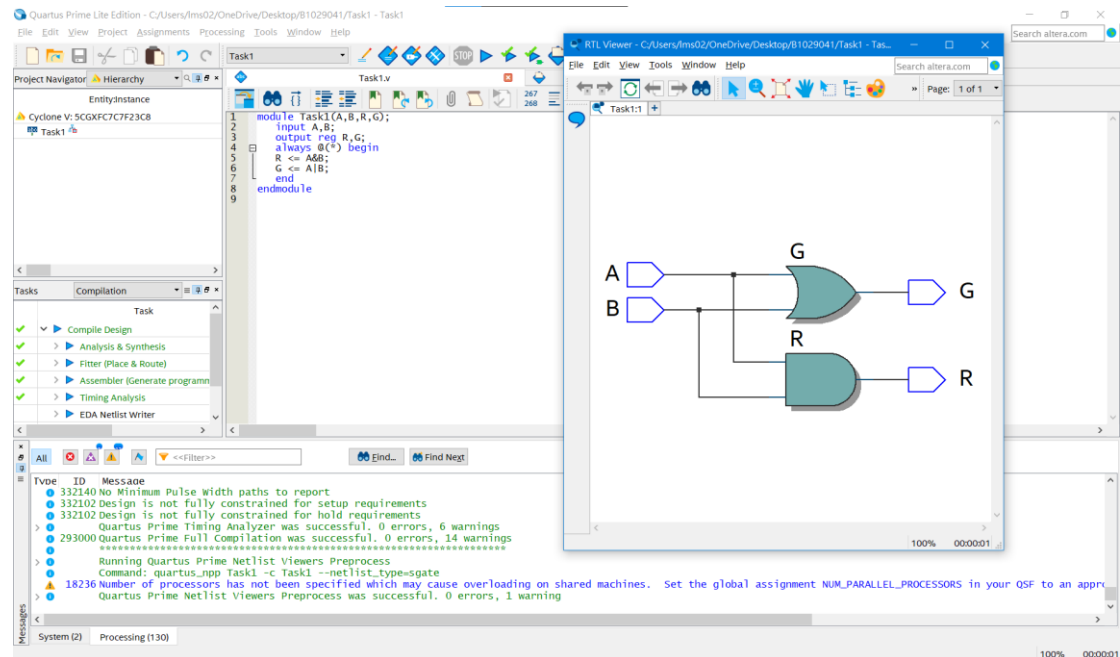


## Perlab02 B0829002

### Task 01:

In this task we need to make a combinational circuit, that will use the and gate and or gate to show result of 2 button inputs, and the Verilog code module will be always determine the inputs.



### Task 02:

This task will use a decoder to recognize the input value of 3-bits binary number and the different output will lead them to the specific 8 LED lights. In the task will use switch and this module determines also always.

File Edit View Project Assignments Processing Tools Window Help

B0829002\_task03031

Project Navigator Hierarchy

EntityInstance

Cyclone IV E: EP4CE115F29C7

task0302

Tasks

Compilation

Task

```
1 module task0302( swi, led);
2   input [2:0] swi;
3   output [7:0] led;
4   reg [7:0] led;
5
6   always @(*)begin
7     led=8'd0;
8     case (swi)
9       3'b000: led[0]=1'b1;
10      3'b001: led[1]=1'b1;
11      3'b010: led[2]=1'b1;
12      3'b011: led[3]=1'b1;
13      3'b100: led[4]=1'b1;
14      3'b101: led[5]=1'b1;
15      3'b110: led[6]=1'b1;
16      3'b111: led[7]=1'b1;
17      default: led=8'd0;
18    endcase
19  end
20 endmodule
```

Find

Find:  List

Look in: sk0302 ... Options...

☒ Include subtities

Find result


Decoder0

swi[2..0] IN[2..0] OUT[7..0] led[7..0]

Compilation Report - B0829002\_task03031


267  
268


332154 The derive\_clock\_uncertainty command did not apply clock uncertainty to any clock-to-clock transfers.  
332140 No Setup paths to report  
332140 No Hold paths to report  
332140 No Recovery paths to report  
332140 No Removal paths to report  
332140 No Minimum Pulse Width paths to report  
332102 Design is not fully constrained for setup requirements  
332102 Design is not fully constrained for hold requirements  
Quartus Prime Timing Analyzer was successful. 0 errors, 5 warnings  
293000 Quartus Prime Full Compilation was successful. 0 errors, 17 warnings

 
 
### Task 03:

This task is a little bit different with the last 2 tasks. This task needs to use the clock to turn the output lighting every second on and off, thus we need to check the frequency of the cpu in the FPGA plate. And then we have to calculate the clock ticks per second is  $5 \times 10^7$  times per second, so we need a counter to record the clock ticks and make sure the clock ticks will be reset to 0 after  $5 \times 10^7$  and the output will be complement.



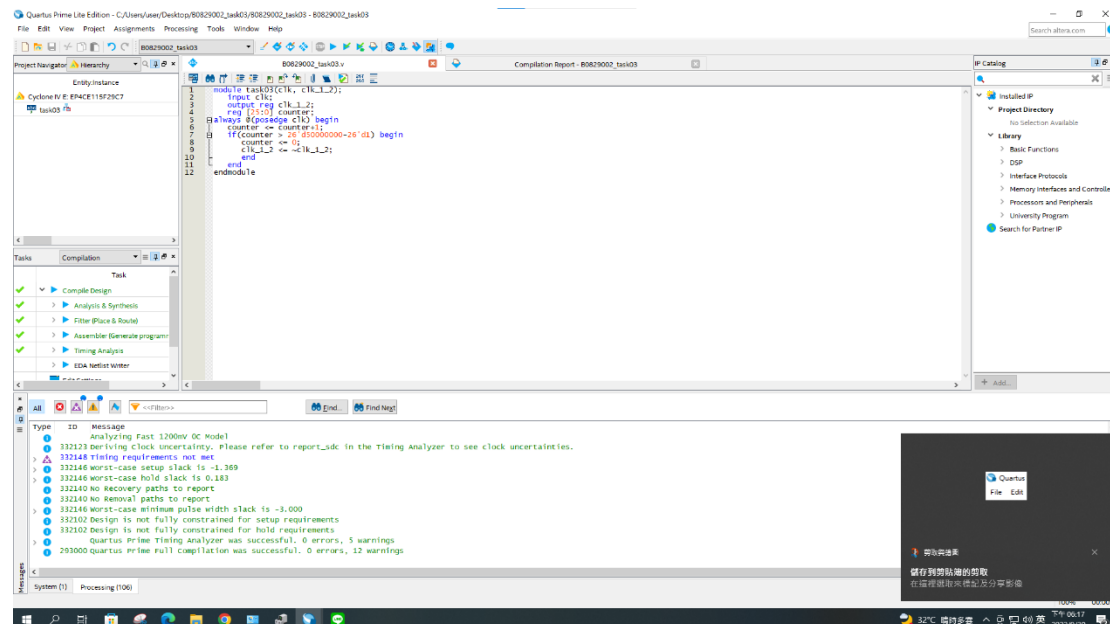

After this lab, I have learned a lot of thing about sequential circuit and the using about clock. In the first task, we finish a simple combinational circuit using AND and OR gates, that trained me to setting the pin on FPGA Plate. And the second task is to make a 3x8 decoder using switch to input signals and we need to plan more pin for the led output and switch inputs. The third task, which I think is the most difficult task in this lab, is using the clock to make a sequential circuit with a output led lighting, which complement the value each second. In this task, the part full of challenge is to divide the clock from  $5 \times 10^7$  to 1 per second, thus we need a counter to count the ticks after each clock trigger ,and after  $5 \times 10^7$  times the counter will be reset and the output signal will also be complemented.